

initial circuit design

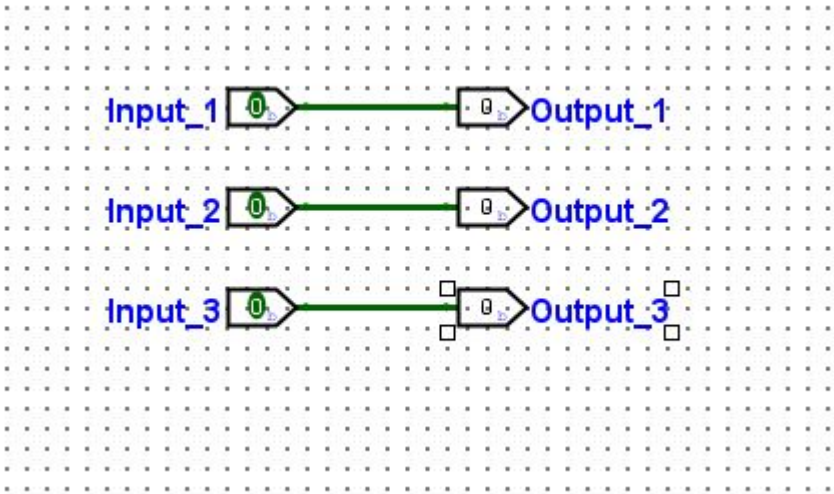


3 inputs that control the 3 segments of the LED, red green and blue

independent circuit design

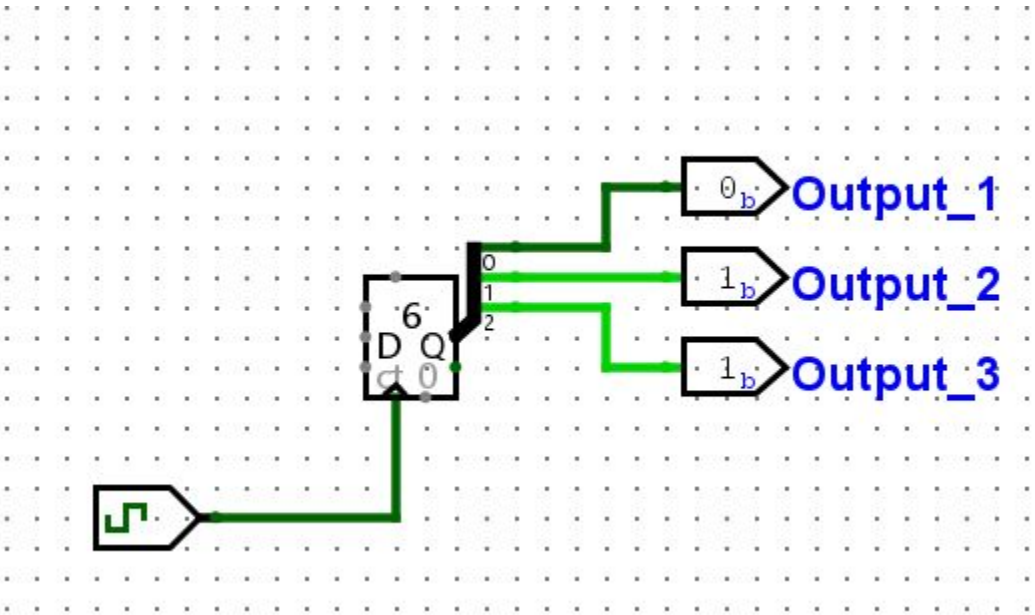


cycles through 8 different combinations on a clock without input

3-input blinking light design

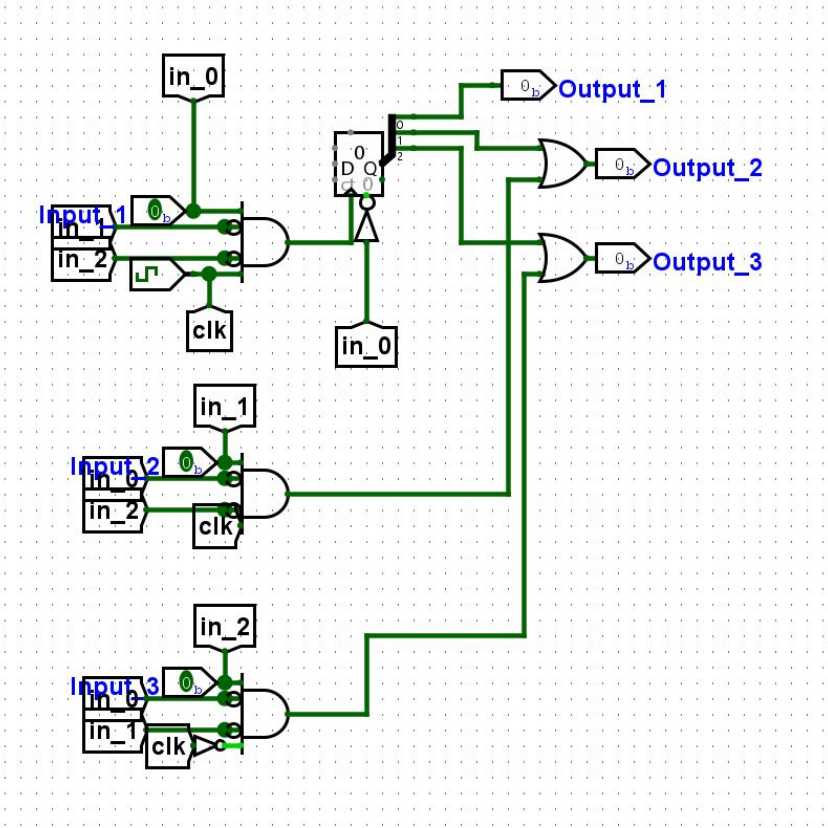


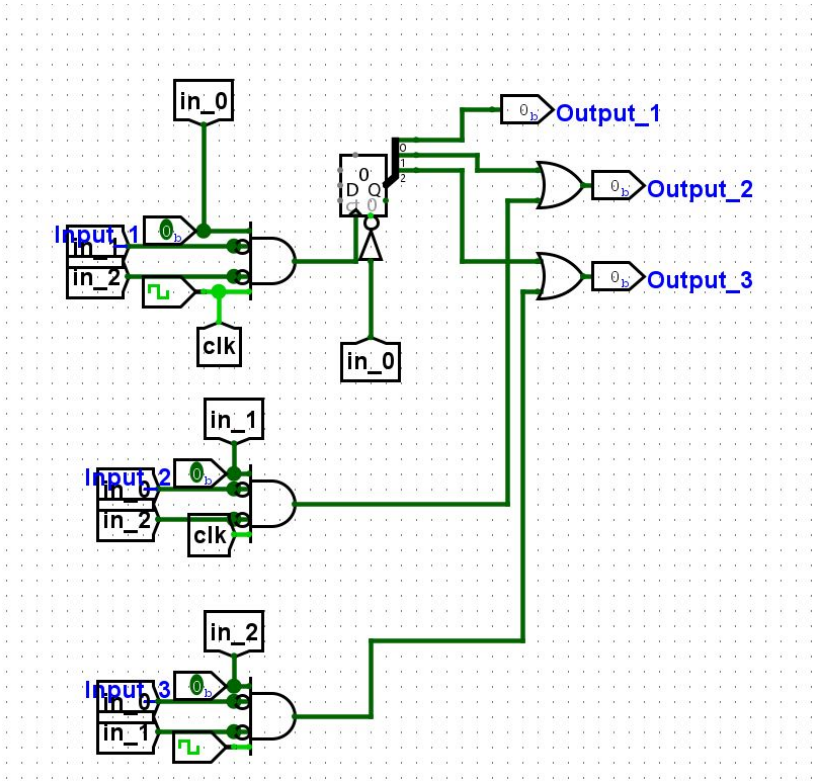
3 switches control from the 8-color pattern, the green blinking pattern and red blinking pattern but red and green go at the same speed



Clock (410,750)	
FPGA supported	Supported
Facing	→ East
High Duration	2 Ticks
Low Duration	2 Ticks
Phase Offset	0 Ticks
Label	
Label Location	← West
Label Font	SansSerif Bold 16
Appearance	Arrow shapes

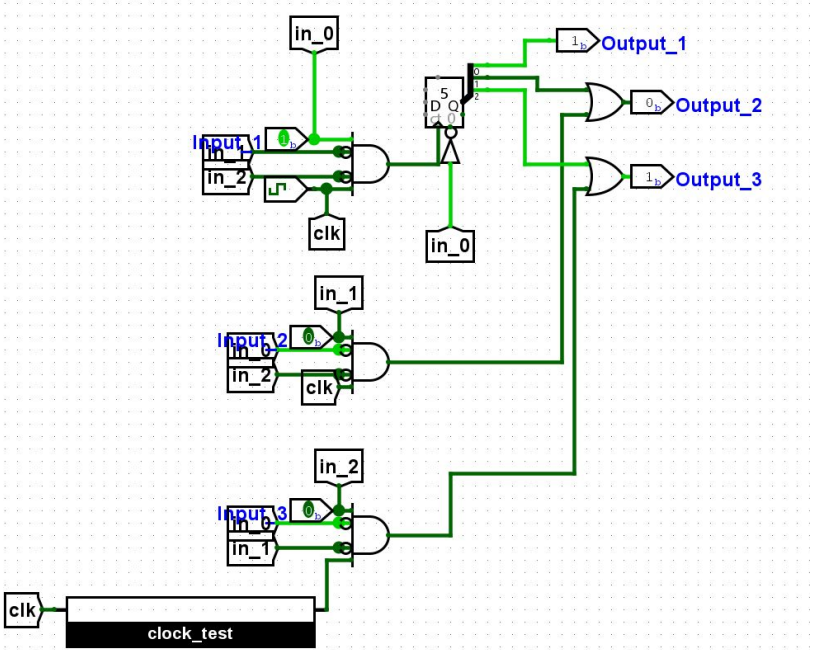added a different clock with a different tick speed at the bottom to make the red light blink at a diff speed



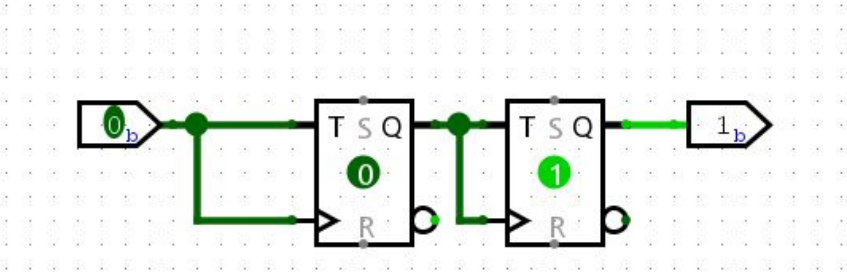

changed that delayed clock to a couple t flip-flops so everything runs on the same global clock