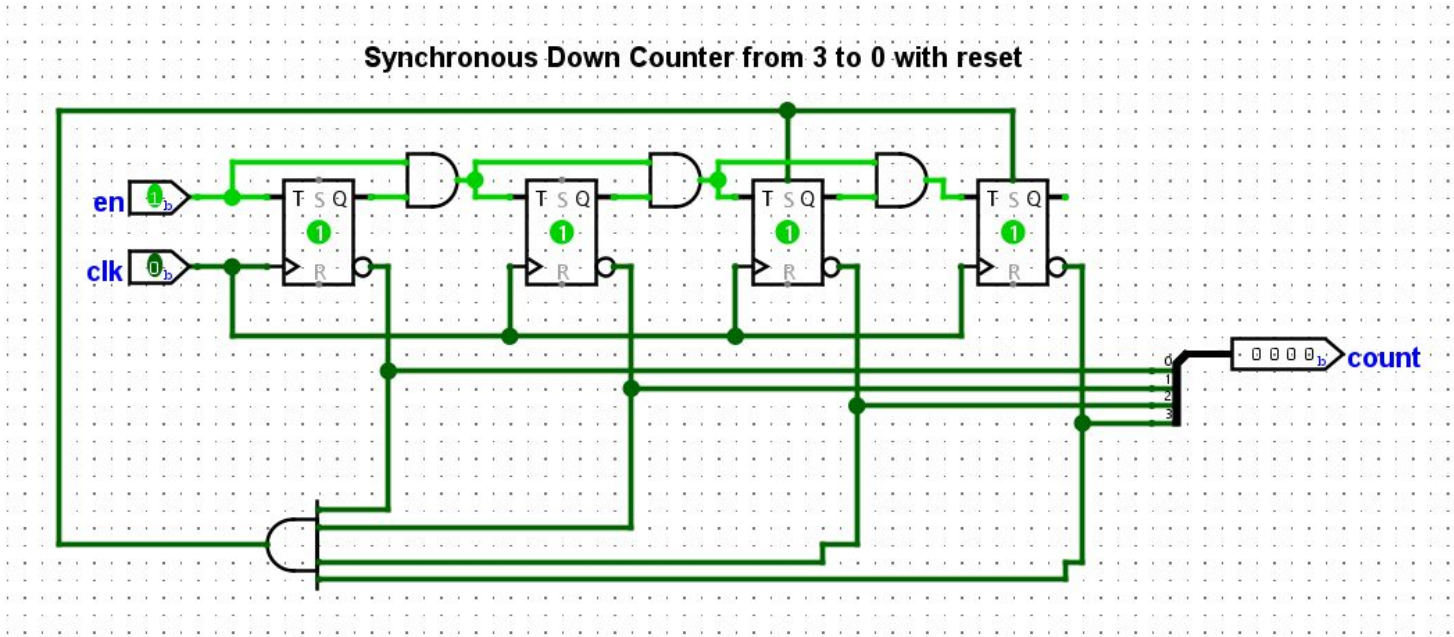
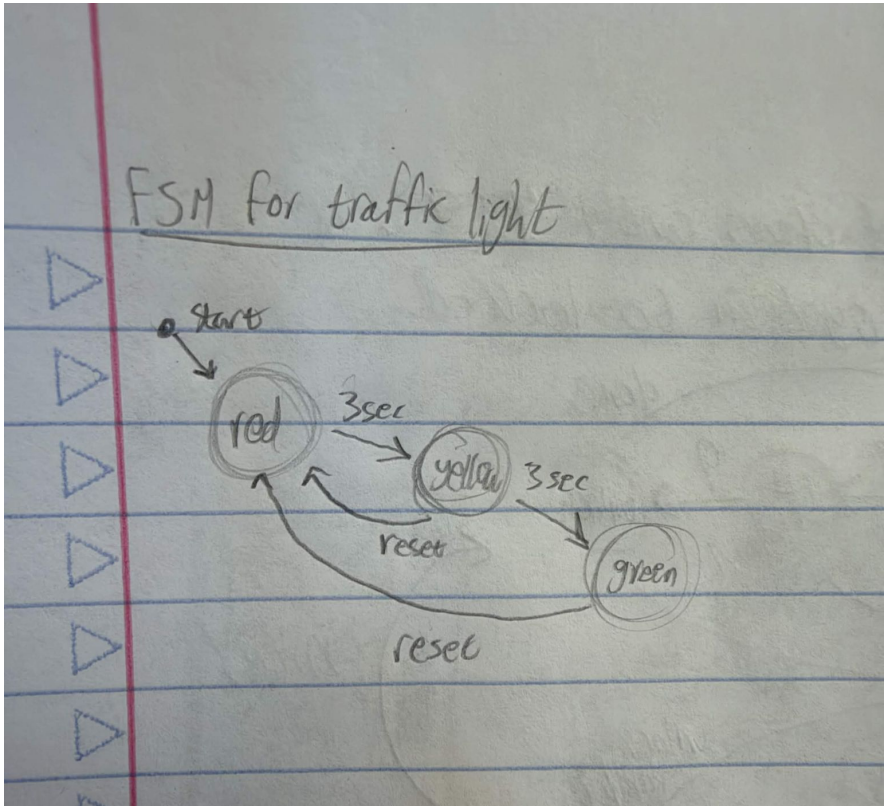
fixed down counter

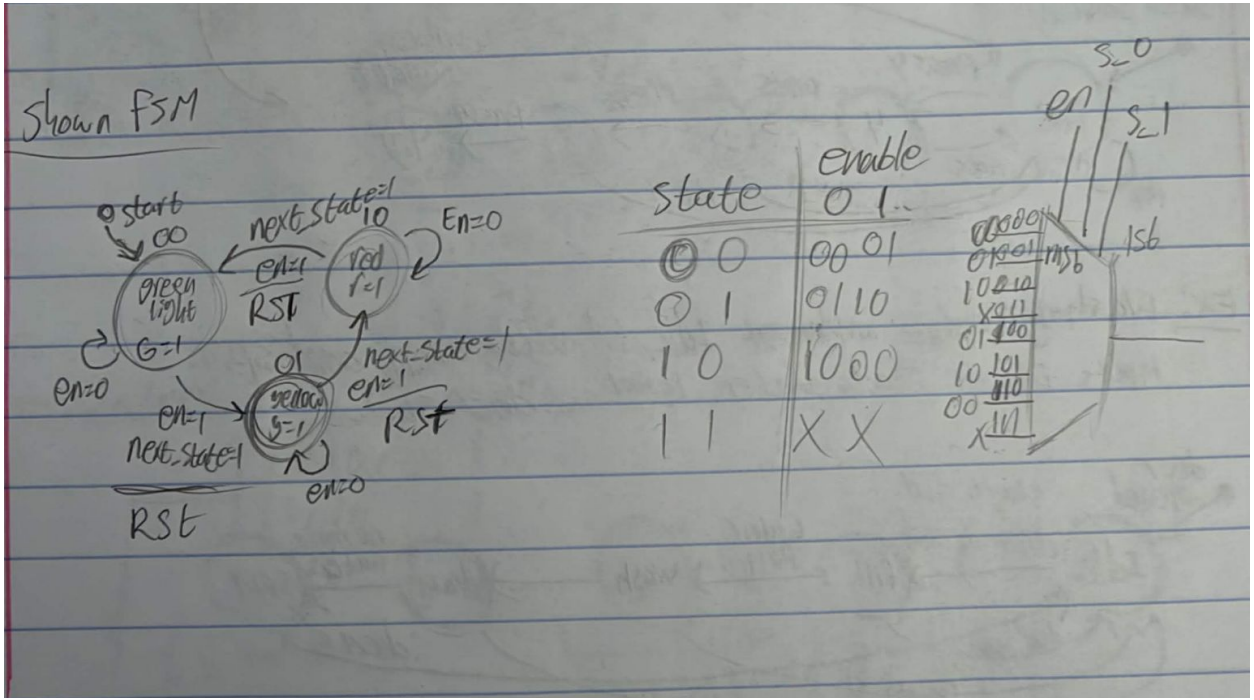


counts from 3 to 0

first fsm

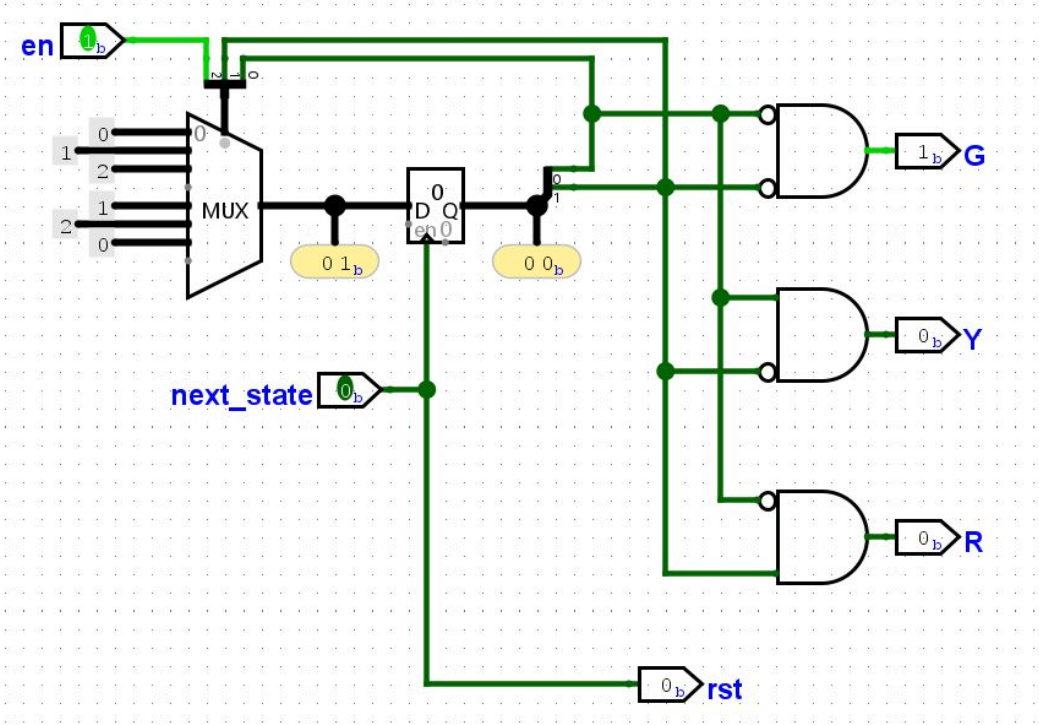

FSM for traffic light
start
red
3sec
yellow
3 sec
reset
green
reset

revised fsm

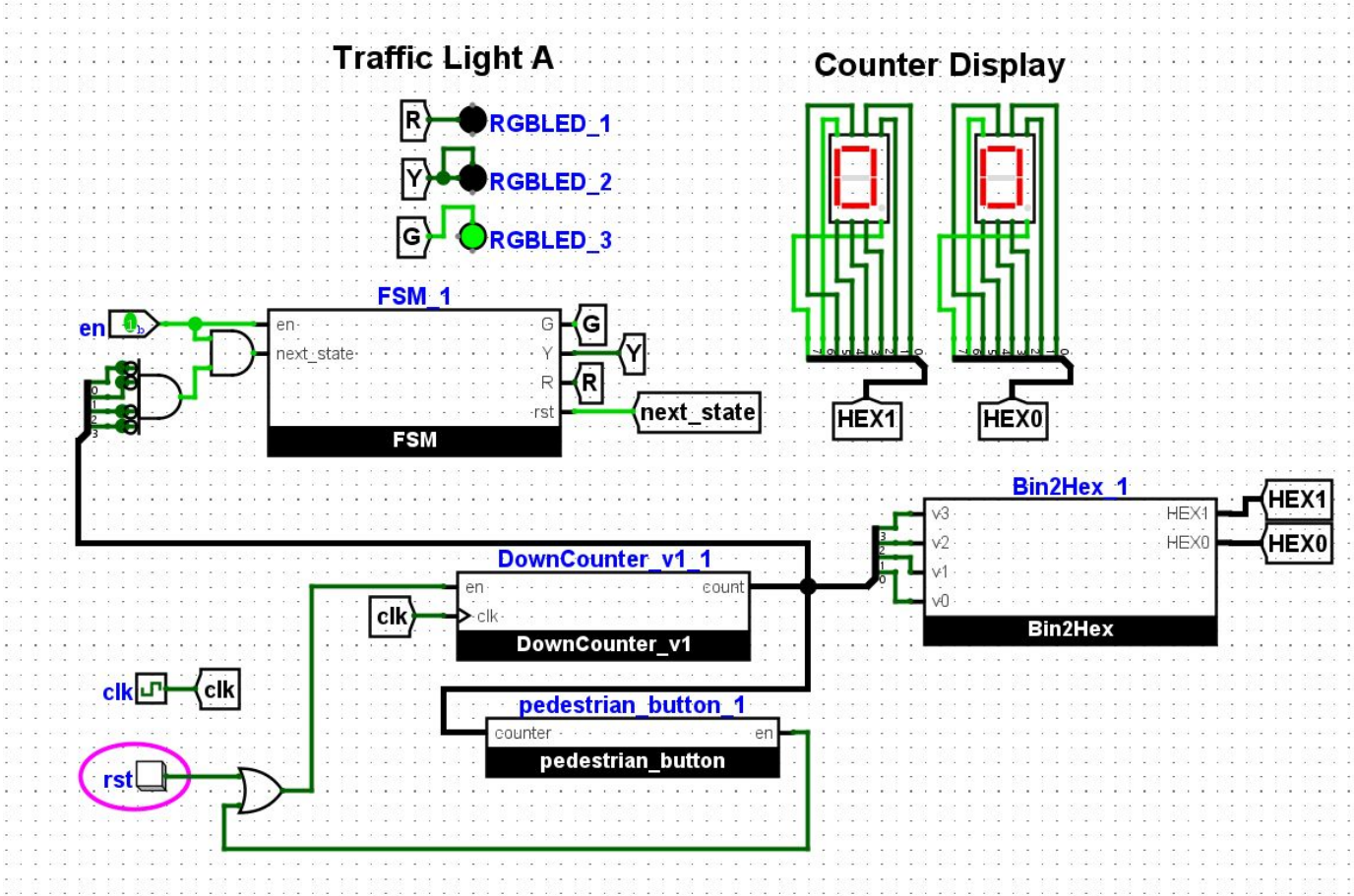


added a truth table and multiplexer to connect with the revised fsm

revised fsm in logisim


en
MUX
D Q
en
next_state
rst
G
Y
R

integration with 3 LEDs


Traffic Light A
Counter Display
R
RGBLED_1
Y
RGBLED_2
G
RGBLED_3
FSM_1
en
next_state
G
Y
R
rst
FSM
next_state
HEX1
HEX0
Bin2Hex_1
v3
v2
v1
v0
HEX1
HEX0
Bin2Hex
HEX1
HEX0
DownCounter_v1_1
en
clk
count
clk
DownCounter_v1
clk
clk
pedestrian_button_1
counter
en
pedestrian_button
rst